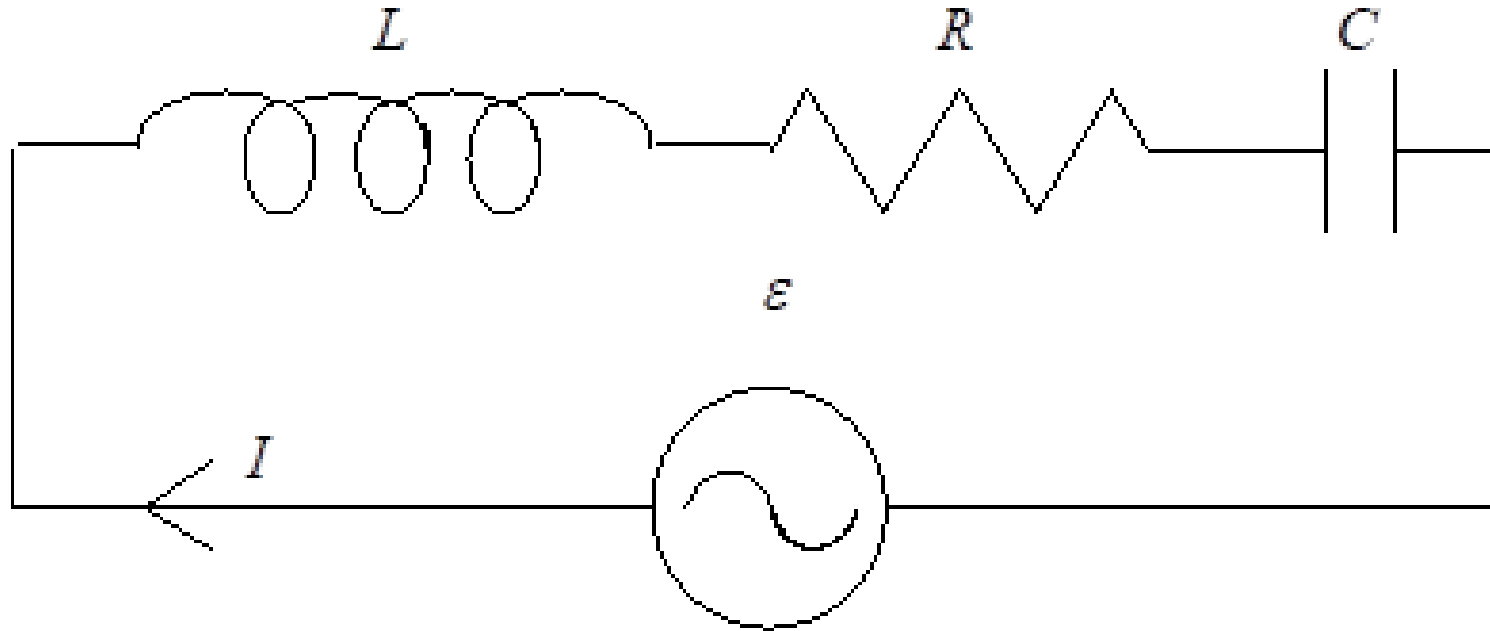


ELEMENTARY APPROACHES TO RLC CIRCUITS

Carl E. Mungan, Physics Department
U.S. Naval Academy, Annapolis MD



Part 1: THEORY



driver: $V_{\varepsilon} = \varepsilon_0 \cos \omega t$ (by choice of zero of time)

response: $I = I_0 \cos(\omega t - \phi)$

responds at
driving frequency

response lags
behind driver

capacitor: $V_C = \frac{Q}{C}$

but the current is $\frac{dQ}{dt} = I_0 \cos(\omega t - \phi)$

so that $\int dQ = \int I_0 \cos(\omega t - \phi) dt$

which integrates to $Q = \frac{I_0}{\omega} \sin(\omega t - \phi)$

and thus $V_C = \frac{I_0}{\omega C} \sin(\omega t - \phi)$

Introduce reactance $X_C = \frac{1}{\omega C}$ to get $V_C = I_0 X_C \sin(\omega t - \phi)$

inductor: $V_L = L \frac{dI}{dt} = -L\omega I_0 \sin(\omega t - \phi)$

introduce reactance $X_L = \omega L$ to get $V_L = -I_0 X_L \sin(\omega t - \phi)$

resistor: $V_R = IR$

so that $V_R = I_0 R \cos(\omega t - \phi)$

emf: introduce impedance $Z = \frac{\varepsilon_0}{I_0}$

so that $V_\varepsilon = I_0 Z \cos \omega t$

$$V_C = I_0 X_C \sin(\omega t - \phi)$$

$$V_L = -I_0 X_L \sin(\omega t - \phi)$$

$$V_R = I_0 R \cos(\omega t - \phi)$$

Now use the voltage loop rule: $V_\varepsilon = V_R + V_L + V_C$

and divide by I_0 to get

$$Z \cos \omega t = R \cos(\omega t - \phi) - (X_L - X_C) \sin(\omega t - \phi)$$

The two unknowns Z and ϕ are to be expressed in terms of the givens L , R , C , ε_0 , and ω .


$$Z \cos \omega t = R \cos(\omega t - \phi) - (X_L - X_C) \sin(\omega t - \phi)$$


Solve by substituting two orthogonal values of t :

$$\omega t = \phi \quad \Rightarrow \quad Z \cos \phi = R$$

$$\omega t = \phi - \frac{\pi}{2} \quad \Rightarrow \quad Z \sin \phi = X_L - X_C$$

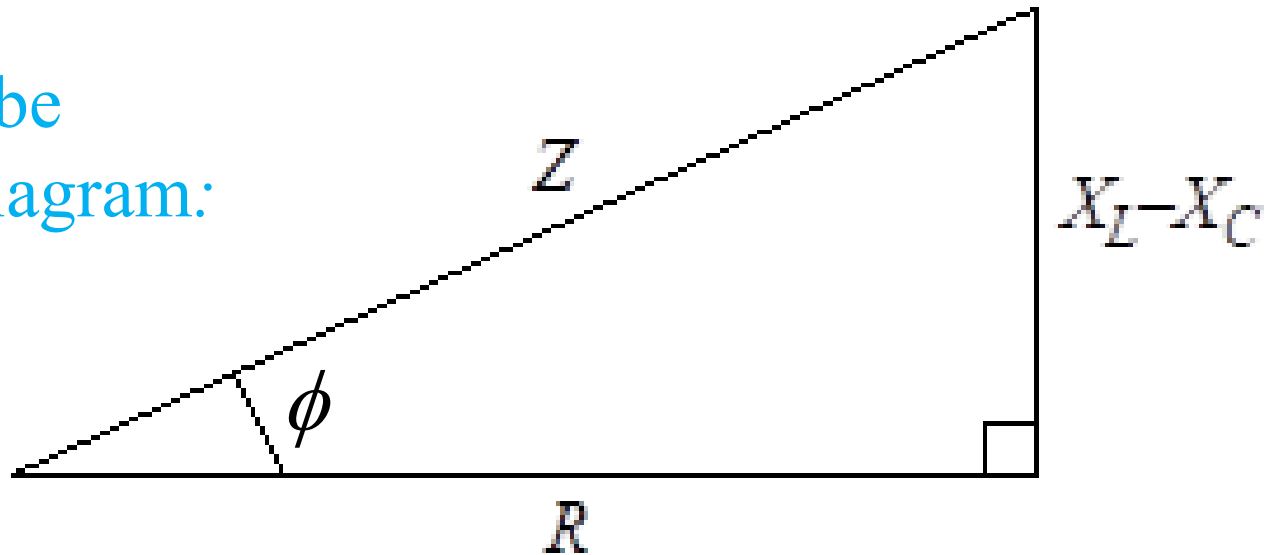These two results can be summarized on a triangle diagram:



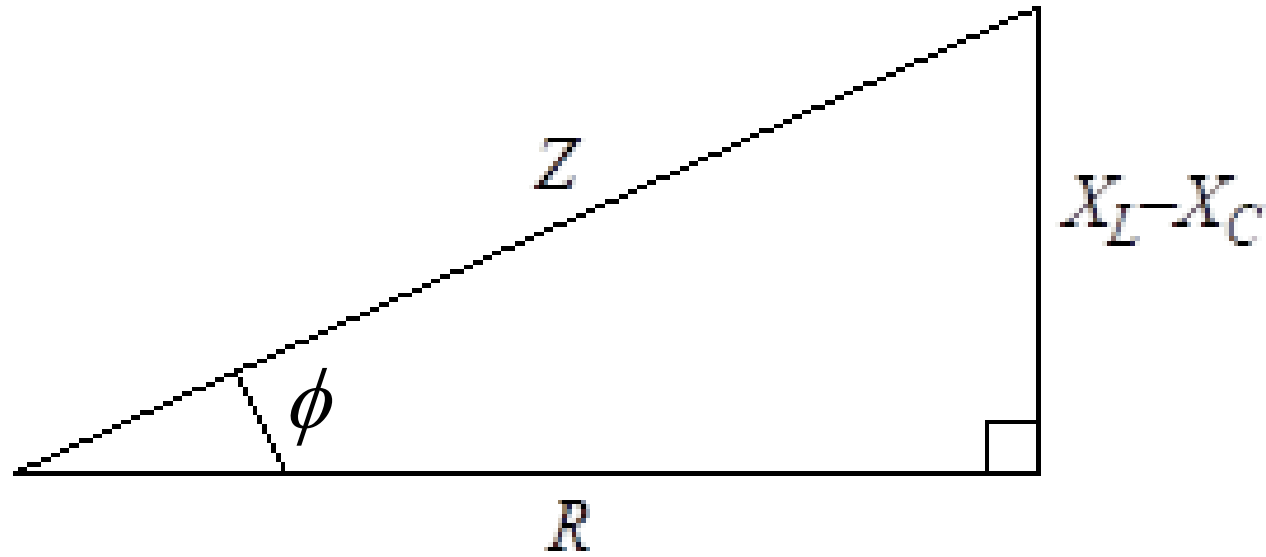


This triangle implies:

the impedance is $Z = \sqrt{R^2 + (X_L - X_C)^2}$

and the phase shift is $\phi = \tan^{-1} \frac{X_L - X_C}{R}$


So we can graph the amplitude and phase shift of the response:

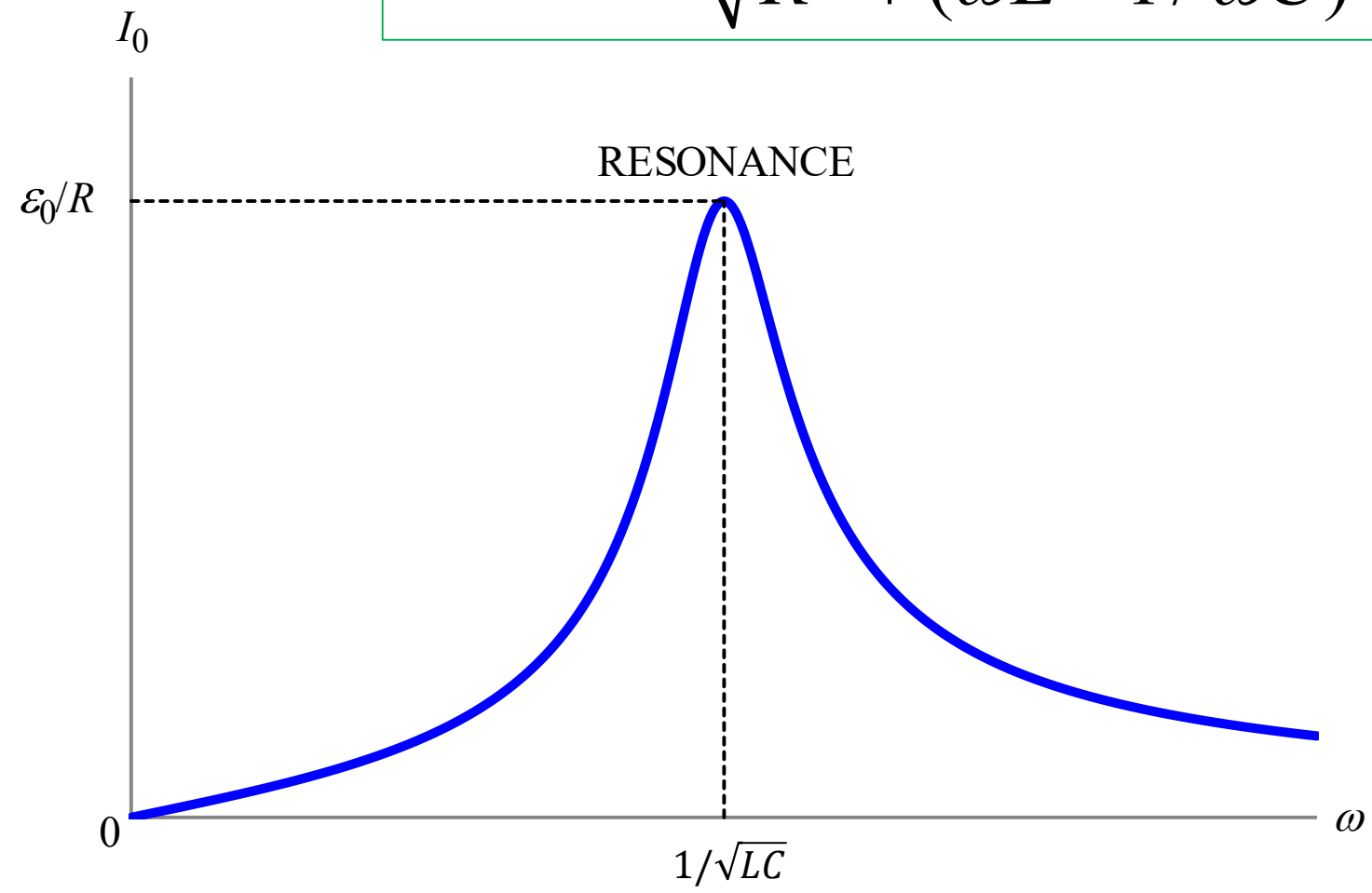current amplitude $I_0 = \frac{\varepsilon_0}{Z} = \frac{\varepsilon_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$




phase lag of the current
relative to the emf

$$\phi = \tan^{-1} \frac{\omega L - 1 / \omega C}{R}$$

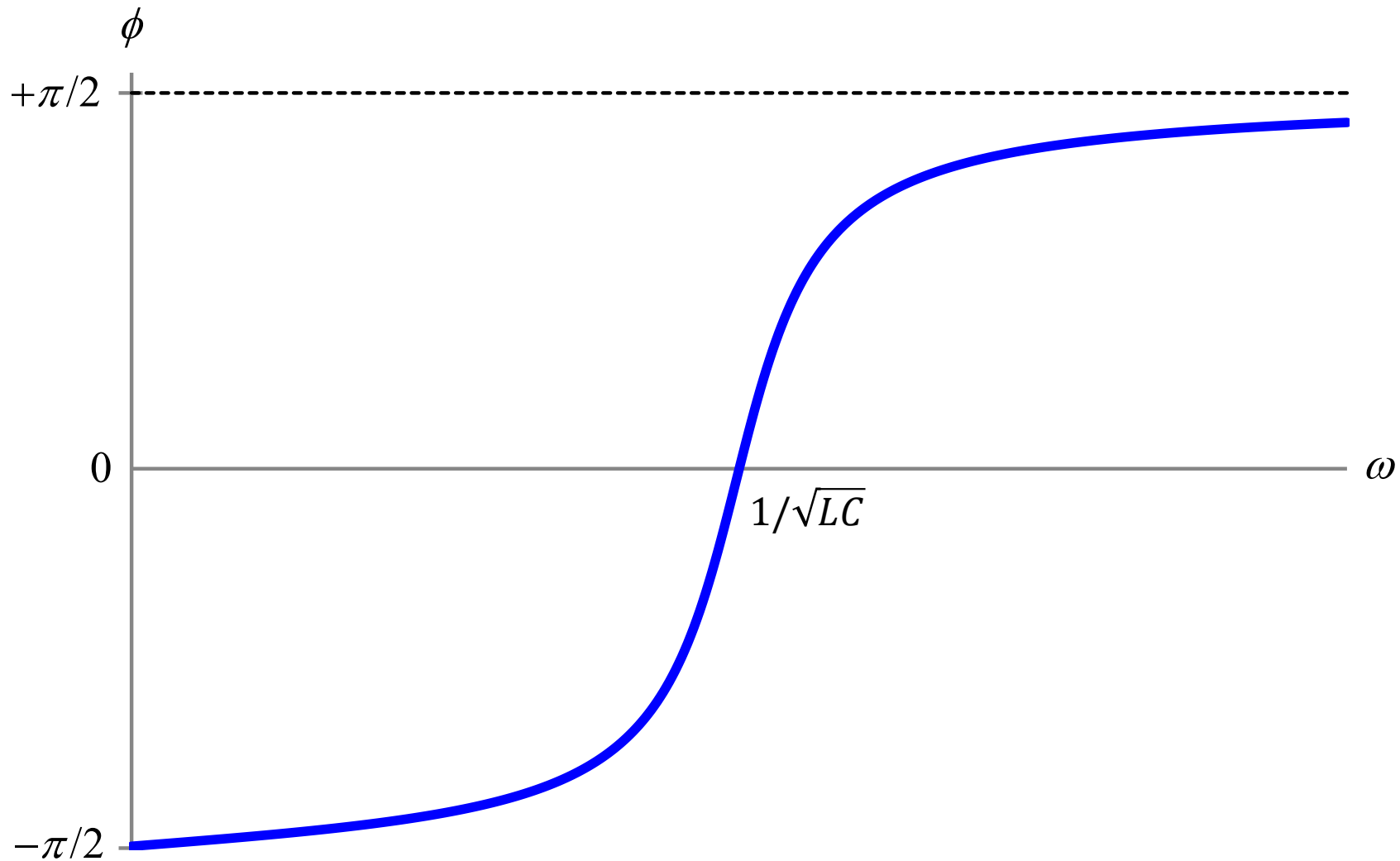



Part 2: EXPERIMENT

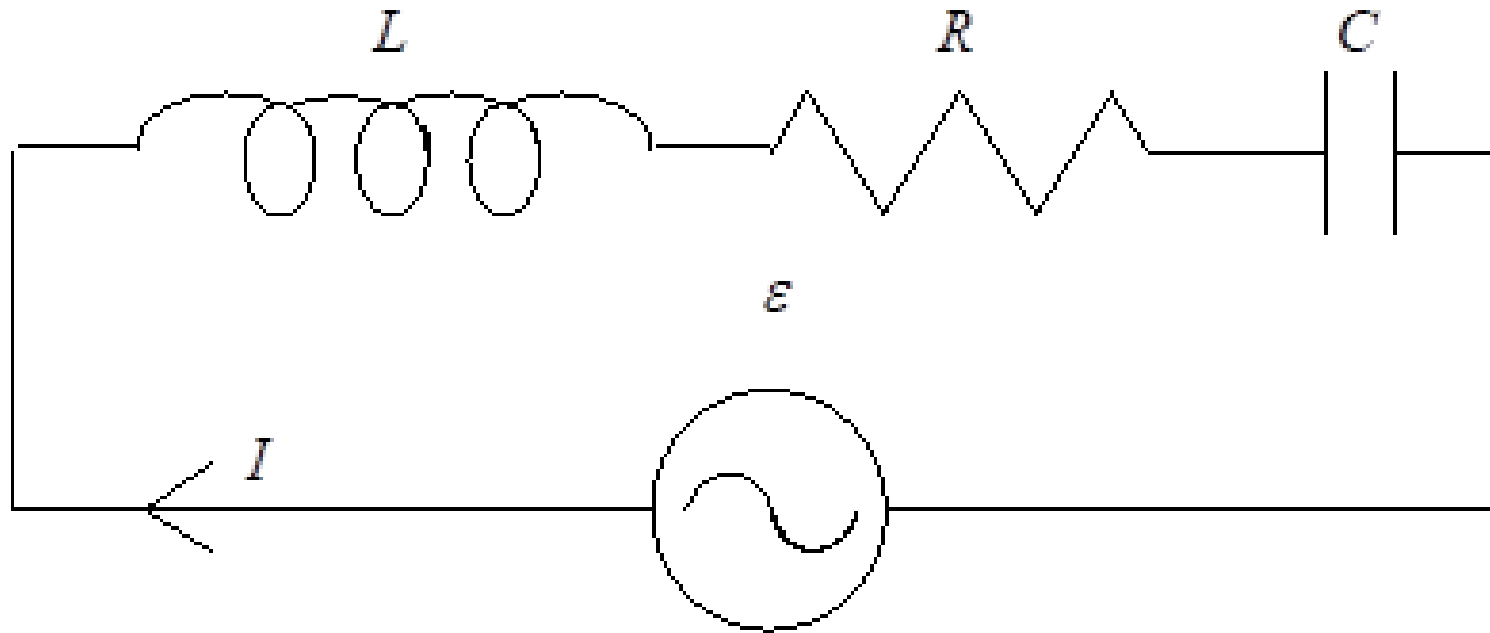

- use large coil for L and R
- use sinusoidal function generator for ε
- use variable capacitor box for C
- use multimeter for measurements

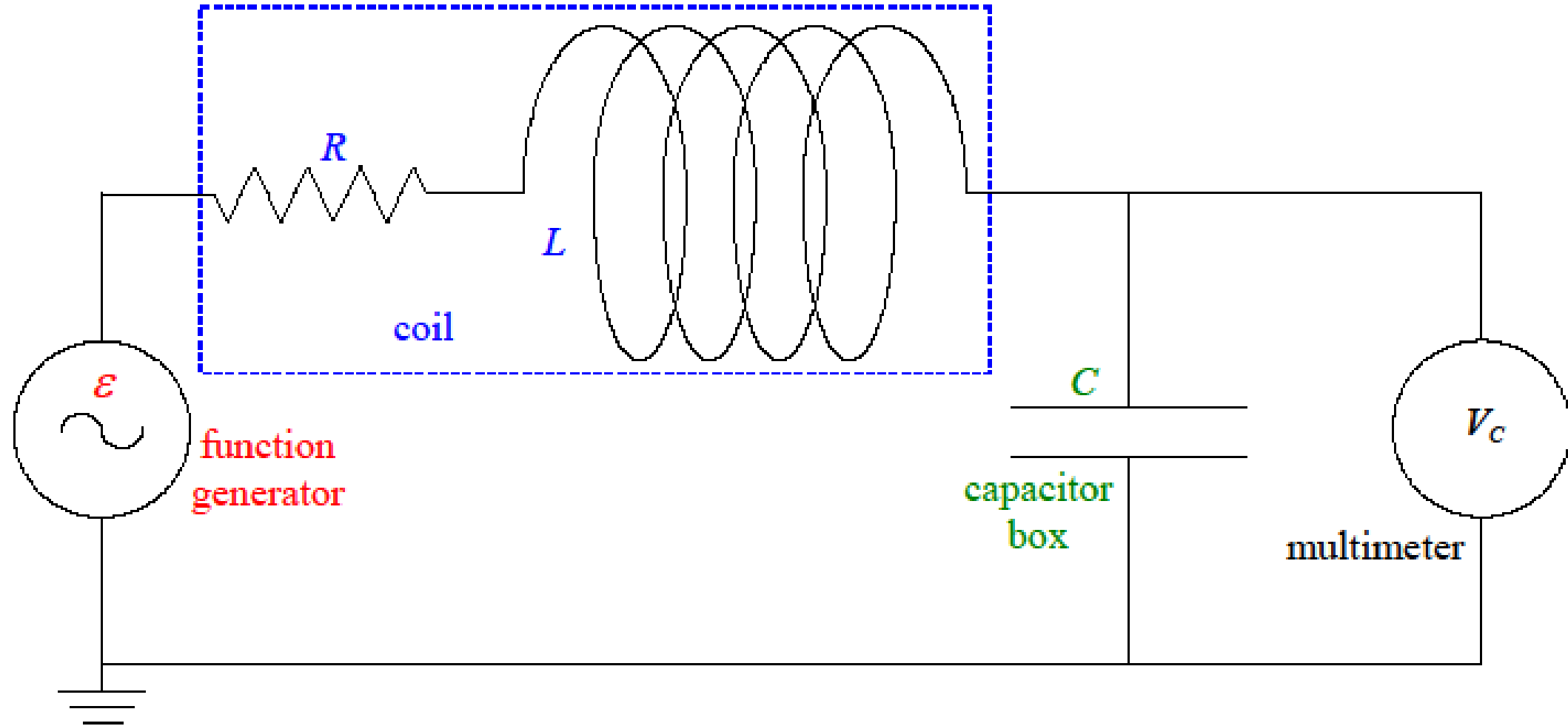Actual circuit configured to measure rms capacitor voltage:



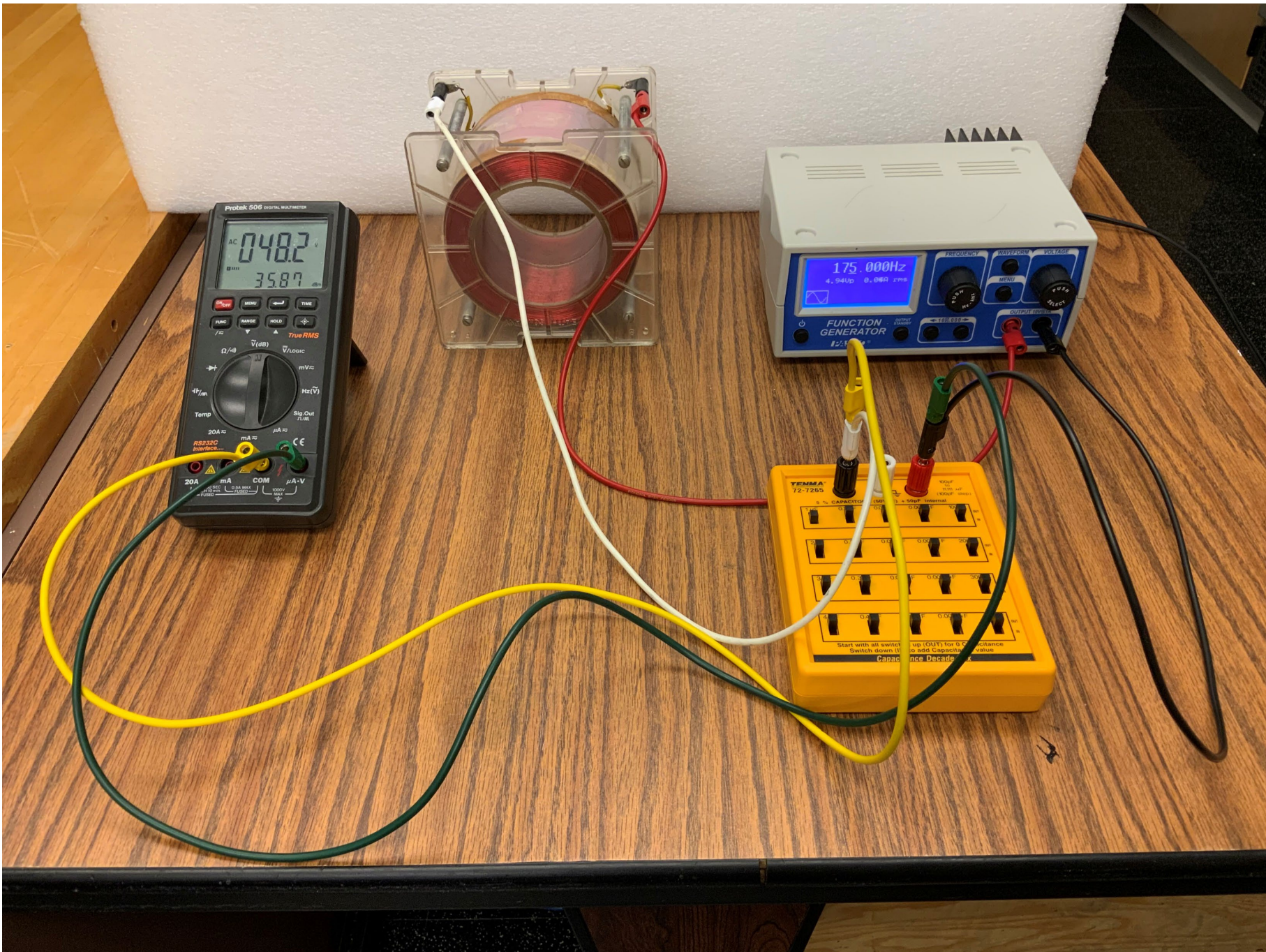

During setup, use the Protek multimeter to measure:

- $L = 0.83 \text{ H}$

- $C = 0.98 \text{ } \mu\text{F}$


so the resonance frequency is 176 Hz

- $R = 63 \text{ } \Omega$


- $V_{\mathcal{E}} = 3.5 \text{ V rms}$

and turn the frequency knob on the Pasco function generator in roughly 10 Hz steps.
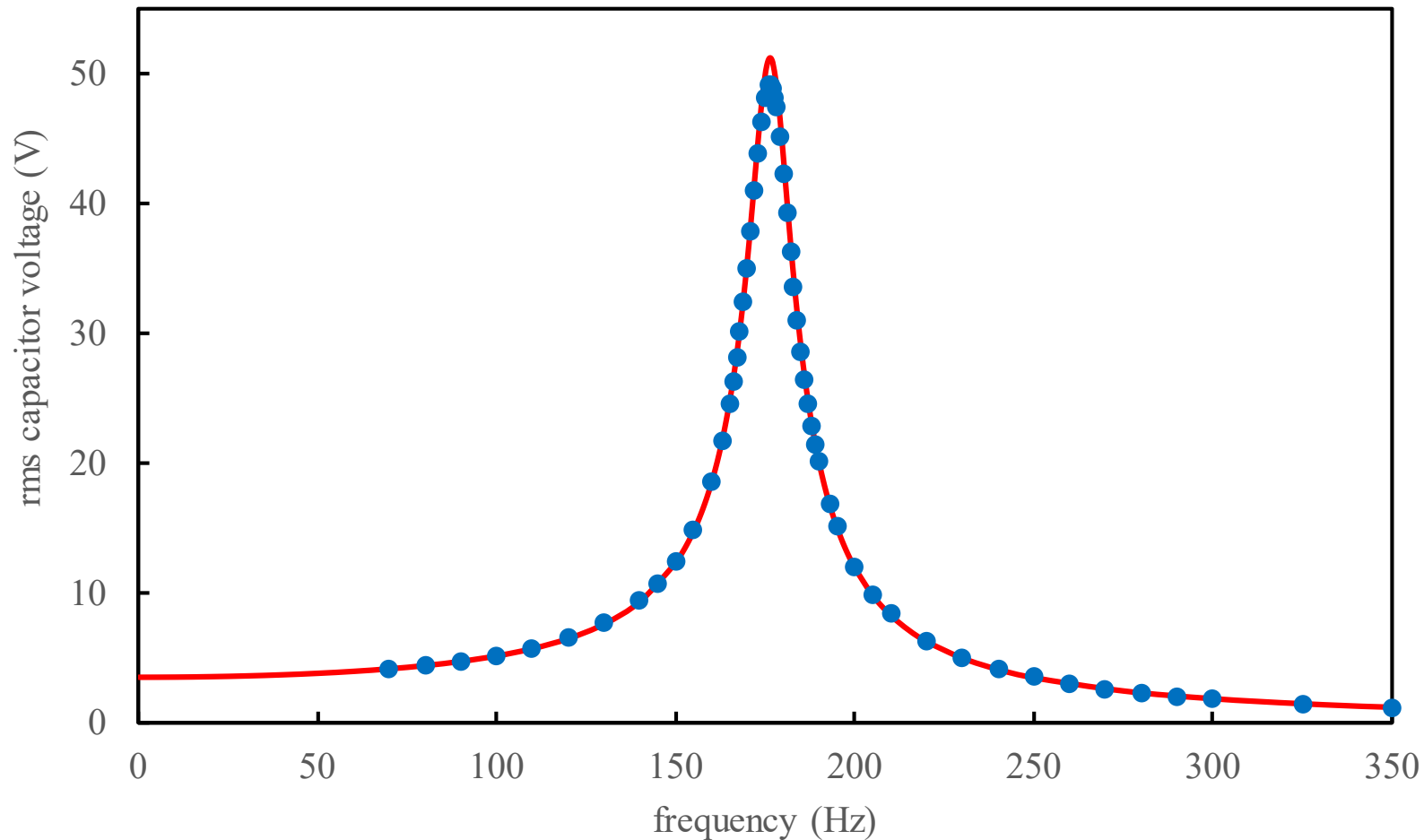
$$\frac{V_{\varepsilon}}{Z} = I = \frac{V_C}{X_C} \Rightarrow V_C = \frac{V_{\varepsilon}}{\sqrt{(2\pi f RC)^2 + (4\pi^2 f^2 LC - 1)^2}}$$



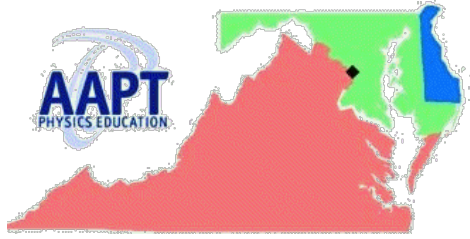Blue data points compared to red theory curve with NO free parameters.



Comments are welcome!



email: mungan@usna.edu

webpage: usna.edu/Users/physics/mungan